

# Intro to Digital Circuits

14 October 2017 14:51

Use DD Flip Flops only

Propagation Delay - time delay between input changing and an output changing

Spec sheets - min max, typical for High-to-Low and Low-to High

Notation -

Number after letter - identify

Number before letter - controlled by the respective input

**Asynchronous - not synchronised to a single clock signal**

**Synchronous - circuit function is synchronised to a single clock signal**

Sequential - output follows a defined sequence

Ripple counter - propagation delay proportional to amount of D FF  
(uses more than one 'clock' signal)


Synchronous counter - constant propagation delay, not bound to amount of D FF

# Introduction to FPGAs

15 October 2017 19:13
 
## FPGA:

- Logic Block
  - Uses LUT to implement logic
  - Has both async and sync outputs
  - Special circuits to combine logic blocks
  - LUT:




Screen clipping taken: 15/10/2017 19:24

- D FF stores value from Bitstream configuration
    - Four levels of 2x1 Multiplexers
    - Can now implement any Boolean expression with 4 inputs - shown above

- Routing Channels
  - Switch blocks (Xilinx)
    - Programmable switches to choose wiring at cross section

 Each wire segment can be connected in one of many ways:




- Switches are n-channel transistors
    - Default OFF - 0
    - Can turn ON (1) from reading a 1-bit configuration register

## I/O Pad

- Configuration:
  - Occurs during power-up
  - Store on local flash memory or DL from a computer
  - Bitstream - contains configuration
    - Configures LUT
    - Configures Switch Blocks
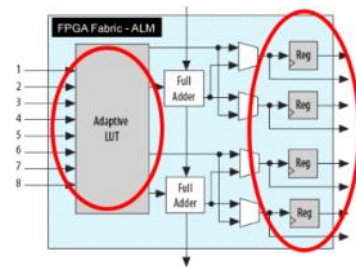
## Cyclone V - FPGA - Adaptive Logic Module - ALM

- Implement:
  - Much larger function vs a 4 input LUT
  - A number of smaller functions




Screen clipping taken: 15/10/2017 19:30

## Features of ALM:

- 8 inputs
- 4 outputs - async and sync
- Be used as a 2-bit full adder
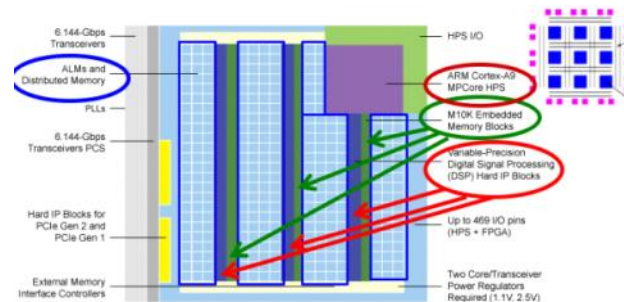
## Cyclone V - Chip-level Structure - SoC



## Also on the chip:

- Over 4Mbit embedded memory
- 87 DSP blocks - useful for multiplication - VARIABLE precision
- Dual-core ARM processor - Cortex A9
- Dedicated hard-logic to connect to PCIe devices and external memory (RAM)

## Tools for Lab - DE1 - (VERI)

- Altera Quartus Prime
- Free web edition
  - <http://dl.altera.com/?edition=lite>

# Verilog HDL

20 October 2017 19:35

HDL - Hardware Description Language

Assign - **continuous assignment** - immediate changes to value

order of assign does not matter

Always / initial - **procedural assignments**

sensitivity list - **always @\*** / @()

when to run body

- **posedge clk - synchronous**

▪ generates D FF

order matters - sequential execution

**reg** - declare variable holds an output

Operators:

bit-wise

bit-by-bit

logical

Boolean value - true or false

reduction

applies operator to elements of an array / bus

wire

used to make inner-connections (non I/O)

**Notation:**

1'b0

1 - how many bits

b - base of number

0 - number

**Concatenate:**

{buses / bit variable} - become larger bus

## **Non-blocking**

- **<=**
  - procedural
- **use for sequential logic**
- values update at same time

## **Testbench**

instantiate a module

initial

begin

**test \*\*\***

end

end

- **\*\*\* - #<time>** - time to change values for test
  - e.g. #50

C syntax:

y = x ? a : b

if x TRUE

y = a

if x FALSE

y = b

case (x)

1'b0: y = a;

1'b1: y = b;

**default:** y = 1;

endcase

- default - safety - catches all unspecified cases

# Counters & Shift Registers

29 October 2017 17:46

## Synchronous Counter

- always
  - `count <= count + 1'b1;`
- synchronous reset
  - `if(rst == 0) // active low`
    - `count <= 4'b0`
  - else
    - `count <= count + 1'b1`

## Eliminate Glitches

- D FF the output - read from D FF
  - vital for control signals
- In Verilog,
  - assign **output inside always** scope

## Timer - prescale clock

- Counts down from N to 0
  - lasts **N+1 cycles**
- output pulse at counter == 0
- uses a down counter; form N to 0
  - hence N+1 cycles per tick

## Clock Divider

- divides input clock by  $2^{*(K+1)}$
- count how many cycles until to invert output
  - ▶ initially 0

## Shift Registers

- D FF
  - connected in serial
- can use to convert a serial input
  - into N bit parallel signal, with N D FF

## Pseudo Random Counter

- linear feedback shift register
  - input to first D FF is:
    - expression of some of the FF outputs

$m$		$m$	
3	$1 + X + X^3$	14	$1 + X + X^6 + X^{10} + X^{14}$
4	$1 + X + X^4$	15	$1 + X + X^{15}$
5	$1 + X^2 + X^5$	16	$1 + X + X^3 + X^{12} + X^{16}$
6	$1 + X + X^6$	17	$1 + X^3 + X^{17}$
7	$1 + X^3 + X^7$	18	$1 + X^7 + X^{18}$
8	$1 + X^2 + X^3 + X^4 + X^8$	19	$1 + X + X^2 + X^5 + X^{19}$
9	$1 + X^4 + X^9$	20	$1 + X^3 + X^{20}$
10	$1 + X^3 + X^{10}$	21	$1 + X^2 + X^{21}$
11	$1 + X^2 + X^{11}$	22	$1 + X + X^{22}$
12	$1 + X + X^4 + X^6 + X^{12}$	23	$1 + X^5 + X^{23}$
13	$1 + X + X^3 + X^4 + X^{13}$	24	$1 + X + X^2 + X^7 + X^{24}$

# FSM Part 1

29 October 2017 17:46

## FSM:

- Inputs, Outputs
- Clock
- Register - stores current state
- Combinatorial Logic - produces next state and outputs

## State Table:

- List states in left column
- Inputs - **one column per bit**
- **Data - State/Output**

## State Diagram:

- Arrows
  - labels - input conditions
  - no label - unconditional transitions
  - omit same state transitions - less clutter
  - can also have input/output
    - output applies to state emitting arrow
    - notation change only
- State Bubbles
  - **label states in decimal**
  - output signals - Boolean expressions inside

## Timing Diagrams

- determined by
  - initial state
  - input signal waveform
- find out state sequence
  - next state depends on input just before clock
- output
  - defined by the expression of the current state
  - **Moore machine**
    - output expressions are just 0 or 1
  - **Mealy machine**
    - expression can involve any input
    - **output can change in the middle of a state**

## Output Glitches:

- likely if
  - two or more state bits change
  - output has same value in both states of a transition

# FSM Part 2

31 October 2017 20:35

## Moore FSM

- no output glitches
- may have one cycle delay on output - due to D FF

## Mealey FSM

- no D FF on output - direct from combinational circuit
- prone to glitches

## FSM Verilog:

- Declarations
- State Transitions [ always @ (posedge clk) ]
  - check for reset
  - case (state)
    - default: // (do nothing)
- Output Logic [ always @ (\*) ]
  - case (state)

## Assigning State Numbers:

- affects circuit complexity
  - one bit changing in transition - simplifies logic
- can use **one-hot** encoding
  - only one bit HIGH
  - for N states - need N D FF
  - Verilog for One-Hot
    - parameter S\_A = 4'b0001;
    - parameter S\_B = 4'b0010;
    - parameter S\_C = 4'b0100;
    - parameter S\_D = 4'b1000;
    - parameter NSTATE = 4;
  - reg [NSTATE-1:0] state;

# Timing Constraints & Analysis

31 October 2017 20:35

## Threshold Voltages

Voh - drive a HIGH out

Vih - detect a HIGH in

Noise margin = Voh - Vin  
error between driving circuit and input circuit

## D FF

setup time  $t_s$   
STABLE Data BEFORE clock

hold time  $t_h$   
STABLE Data AFTER clock

if broken  
'metastable' state  
2 FF could hold different values for same signal  
solve by using chain of 2 FF

## Timing Constraints:

- never  $t_s$  and  $t_h$  in same inequality
- get two inequalities based from timing inequalities
- for min clock period - max freq:
  - trace back for data and clock signal
  - setup:

- **$\max(\text{data}) + \text{setup} < \min(\text{clock})$**
- **$\max(\text{clock}) + \text{hold} < \min(\text{data})$**

- **if coming from FF, consider prop delay of FF**
- **hold times - checking for when next input can be taken (+T)**


## Synchronous Transmission:

- two systems share same clock
  - there is propagation delay along the wire to 2nd system clock arrives later
  - means each system must operate on different edge of clock
    - not enough time otherwise
  - usually get a pair of timing constraint inequalities for each FF
    - setup and hold inequalities


# Basic DAC

19 November 2017 19:54


## Simple DAC:

 

 - ratio of resistor conductance's represent weighting of binary bit
  - if X bits is large enough, end up with **very large resistors**
    - vary line voltage values and use smaller resistor**
    - base on bit weighting
- high resistor values -> high output impedance
- low resistor values -> high current draw
  - solution is to add op-amp



 - low output impedance, but
  - slow, limited by slew rate**
  - hard to get suitable resistors for high bit DAC's
- Using a reference voltage



- X0..3 controls switches
  - connect Vref to respective resistors in network

Jargon: expressed as multiple of  $\Delta V = 1 \text{ LSB}$

Nominal Line - perfect linear line

- Resolution**:  $\frac{\text{voltage range}}{2^N}$  for N-bit DAC
- Accuracy**: max error from reference line
- Linearity**: max error from new line with same gradient as nominal line
- Differential Linearity: worst error from X->X+1 - measure smoothness
- Monotonic**:  $V_{OUT}$  always increases as input steps higher
- Settling Time: time taken to reach final value within some tolerance as input changes

## Digital Attenuator:


- instead of  $V_{ref}$ ,  $V_{IN}$
- digital input controls amount  $V_{IN}$  is multiplied by
- called a *multiplying DAC*



## More DAC's

06 January 2018 20:38

### DAC using Resistor String

 

N-bit to  $2^N$ -bit decoder

- output is one-hot encoded, selects one switch to turn on
- Lowest choice is 0V, Voltage splits along string


Pros:

- monotonic
- same R throughout - easy to make
- only two switches change - low output glitch and fast switch

Cons:

- large number of resistors for high N
- large total R- higher noise

Improvement: **Tree of Switches**

 


- still using same resistor network - control is different
- no decoder, input directly controls switches
- LSB controls first layer of switches, MSB last switch

Reduces number of switches from  $N$  to  $\log N$
 
### Bipolar DAC

- uses **offset-binary** notation to output  $\pm$  voltages
  - zero = midpoint
  - **Invert MSB of 2's compliment to convert to offset**
- uses current mirror



### DAC using R-2R Ladder

**Ladder - Voltage out = 0**

- current splits at each junction




- Replace  $2R$  with  $R$ , and add another  $2R-2R$



Can do this repeatedly

**DAC:**

Input current =  $16I_0$

 


- $V_-$  for op-amp remains constant at 0V, so current is weighted in binary powers
- Only  $V_{REF}$  is input to ladder
- use CMOS gates (4) for switch, controlled by input

$$V_{OUT} = -X \left[ \frac{V_{ref}}{2^N R} R_f \right]$$
 
### PWM DAC:

- compare triangular reference signal with input data value
  - triangular value generate by wrap-around counter



COMP outputs HIGH to FF while counter value  $\leq$  REG value (data\_in)

- Pulse Width is **linearly proportional** to value of data\_in

```

module pwm (clk, data_in, load, pwm_out);
    input      clk;           // system clock
    input [9:0] data_in;      // input data for conversion
    input      load;          // high pulse to load register
    output     pwm_out;       // PWM output

    reg [9:0] d;              // internal register
    reg [9:0] count;          // internal 10-bit counter
    reg [9:0] pwm_out;

    always @ (posedge clk)
        if (load == 1'b1) d <= data_in;
    
```

```

initial count = 10'b0;
always @ (posedge clk) begin
    count <= count + 1'b1;
    if (count > d)
        pwm_out <= 1'b0;
    else
        pwm_out <= 1'b1;
end
module
    
```

# ADC

19 November 2017 19:54

Loss of information from ADC.

**Unipolar** - +ve input voltages only  
usually round to **nearest integer** ( $V_{IN} / 1\text{LSBVolts}$ )

Sampling:

- take sample of signal at freq.  $f_{\text{samp}}$
- causes *aliasing*: any freq.  $f$  is indistinguishable from  $kf_{\text{samp}} \pm f$ , for all integer  $k$ 
  - Nyquist limit: contain frequencies below  $\frac{1}{2}f_{\text{samp}}$

Quantisation Noise:


- infinite input range mapped to finite output
- difference between actual and sampled value = noise
  - max =  $\pm 1\text{LSB}$  V

Threshold Voltages:

- $\pm \frac{1}{2}\text{LSB}$  of kLSB
- $2^N - 1$  threshold voltages for an N-bit ADC
- provided by a DAC within the ADC

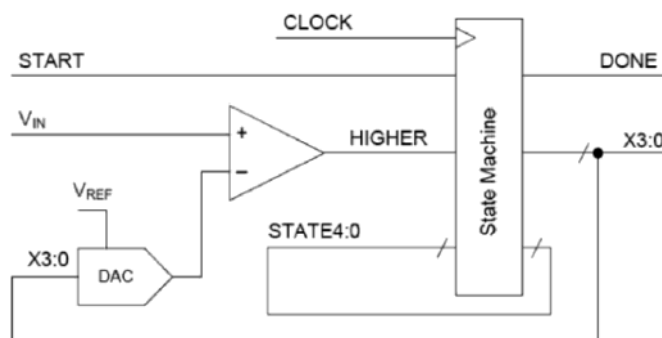
## Successive Approximation ADC:

- only make N comparisons - via binary tree - follow a path
- Test from MSB to LSB, starting with 0b100...0
  - FSM and analogue comparator to determine next state



- Need to sample and hold  $V_{IN}$  still

## Simple Flash ADC:

 


The simplest ADC is the flash ADC. We are converting from the range of 0V to 4V to a digital range of 0 to 7 in binary.

A voltage divider with a string of resistors  $R$  (which is the DAC circuit) is used to provide all the threshold voltages needed - i.e. 0, 0.5, ... 3.5. 7 analogue comparators are used to determine which voltage interval  $V_{IN}$  lies. For example, if  $V_{IN} = 1.75\text{V}$ , then  $G1$  to  $G3$  are logic '1' and  $G4$  to  $G7$  are '0'. This produces the thermometer code which is decoded into a binary number  $X[2:0]$ .
 
## Sample/Hold

- $V_{IN}$  can change during conversion, so have to take a sample and hold the value while conversion takes place
- Choice of Capacitor:
  - big  $C$  - holds voltage longer despite leakage currents
    - but slow acquisition
  - small  $C$  - faster acquisition time - for getting next sample
    - but much more voltage drift




# Memory Interface

09 December 2017 17:27

**sRAM:  $2^N \times M$**  - as square as possible - minimise parasitic capacitances


- N-bit address bus
  - MSBs select row
    - only one row active at a time
  - LSBs select column
    - exploit spatial locality
    - lower power when access same row
- M-bit data bus

 Each bit for M has its own cell array, this array is duplicated for each bit



## Terminology

### 8k x 8 Static RAM

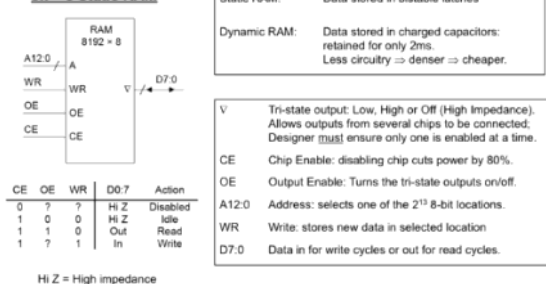

Static RAM: Data stored in bistable latches

Dynamic RAM: Data stored in charged capacitors; retained for only 2ms. Less circuitry  $\Rightarrow$  denser  $\Rightarrow$  cheaper.

V Tri-state output: Low, High or Off (High Impedance). Allows outputs from several chips to be connected. Designer must ensure only one is enabled at a time.

CE Chip Enable: disabling chip cuts power by 80%.

OE Output Enable: Turns the tri-state outputs on/off.

A12:0 Address: selects one of the  $2^{13}$  8-bit locations.

WR Write: stores new data in selected location

D7:0 Data in for write cycles or out for read cycles.

## Timing:

### Read

- **address access time** = time for new data to be ready when address changes for a read
- **output enable access time** = time for data to be driven when OE asserted
- generally, address AT > OE AT

### Setup Times:

- **EACH Microprocessor outputs** to DATA ready
  - includes gate delays and RAM access timing
  - $Gate\ delay + RAM\ access\ time + \mu P\ setup\ time \leq MCLOCK$

### Hold Times:

- only worry about MCLOCK path to DATA changing
- $MCLOCK + Gate\ Delay + OE\ tristate\ delay \geq MCLOCK + \mu P\ hold\ time$

### Write

- address must remain constant at both ends of a write pulse
- input data only matters at end of write pulse
  - has its own setup and hold times
- before going back to read mode, data must be removed from data bus

### Timing:


- Microprocessor control signals, address bus and data bus must meet demands of **WRITE setup and hold times for BOTH rising and falling edges**
- **WRITE pulse width** (from  $\mu P$ ) must also meet memory chip req.

## Microprocessor Memory Mapping:

Address Space is divided to different spaces, ROM, RAM, I/O..

Use separate chips


requires CE decoder

 

requires **control signals to each chip**

**derive from timing diagrams**, output from microprocessor


input signals to memory chip

 

# FPGA Embedded Memory

09 December 2017 17:27


## Register:

 

- **regid** - identify which word in register file
  - select line signals generated using Decoder
  - binary -> **one-hot code** (unary)
- **simplest** form of storage, **really fast**
- in FPGA, **implements using ALM**
  - each ALM has **2 D FF's**
  - $N - \text{bit reg} = \frac{N}{2} \text{ALM} * \# \text{ of words}$
- alternatively, implement using sRAM
  - not as fast, less ALM usage

 
## Internals:

- **2D array of FF with tri-state outputs**
- data bus = BIT bus - bi-directional
  - decide if this word and if write


 
## Memory Blocks on an Cyclone V FPGA

- 397 memory blocks in C5-SE-A5 series
  - each with 10kbits of storage (M10K)
    - width from 1 to 40 bits
      - ◻ e.g. x8 or x10, x16 or x20
      - ◻ extra 2 bits used for parity or tag
    - larger width -> smaller depth
  - operating modes:
    - single-port RAM
      - ◻ simple dual-port - R/W separate ports
      - ◻ Read-During-Write
        - ◆ New Data - read data from write port
        - ◆ Old Data - read old data from address
      - ◻ !Read-During-Write
        - ◆ RAM output retains most recent value
          - ◇ (data from previous address before the write)
    - true dual-port
      - ◻ R/W on both ports
    - shift-register
      - ◻ shift N-bits for M stages
      - ◻ holds M words
        - ◆ 'tap' output - NxM bit - output all data currently inside
      - ◻ input and output is N-bits
    - ROM
      - ◻ can be initialised with a '.mif' file
    - FIFO
      - ◻ implement a queue
      - ◻ **rate match data** producer and consumer



- ◆ After write or read operation, FULL and EMPTY indicate status of buffer.
- ◆ Used by external logic to control own reading from or writing to the buffer.
- ◆ FIFO resets to EMPTY state.

- ◆ Address pointers are used internally to keep next write position and next read position into a dual-port memory.



- ◆ If pointers equal after write => FULL:



- ◆ If pointers equal after read => EMPTY:



# Adders and DSP Block

09 December 2017 17:27

## N-bit ripple carry adder:

- uses Full Adders in serial
- Treat inputs as:
  - unsigned - N+1 bit output (carry out is the +1th bit)
  - 2's compliment signed - N-bit Signed output
- Cyclone V ALM has 2 Full Adders in each one
  - connect ALM's to get larger N-bit adders
  - has dedicated carry chain - fast ripple carry chain

## Delays:

- delay is data-dependant
  - account for initial values of ALL the inputs
  - which input changes
- Worst-Case delay is most important
  - determines max clock speed in a synchronous circuit
- worst case propagation delay in Ripple-Carry Adder
  - $(N - 1)CarryDelay + SumDelay$

## Adder size selection:

- Add two N-bit numbers
- use N+1 adder
  - Zero-extend unsigned
  - Sign-extend signed
  - avoid overflow
  - required for Signed
  - Unsigned could use carry out, but use Sum instead
    - adder works for both

## Shrinking Binary numbers:

- MSB end trivial
- LSB end
  - truncate - chop off
  - round
    - add half LSB of final
    - then truncate
    - e.g. 5-bit to 3-bit
      - add 0b'00010
      - where red is final bits
      - then remove last 2 LSB

## Cyclone V DSP Block:

- multiply-accumulate function
  - value can be used as one input to adder next cycle
- internal coefficient memory
  - store a constant value (useful for FIR filter)
- **configurable multipliers**
  - three 9x9
    - useful for video processing - 8-bit RGB or Grey
  - two 18x18
  - one 27x27
- can feed adder or accumulator in the DSP block
- NxM bit multiply
  - N+M bit product
  - N+M-1 bits if both are 2's compliment signed
    - Sign bit is repeated in MSB (always same as next lower bit)