

Overview - Digital Concepts


13 October 2016 10:27

Exam in Summer Term

Tutorial Questions every lecture - non assessed


15 total lectures

 Binary values are also represented by voltage levels



Major parts of a digital pulse

 - Base line
- Amplitude
- Rise time (t_r)
- Pulse width (t_w)
- Fall time (t_f)



Rise time - 10% to 90%

Fall time - 90% to 10%


Pulse width - rise 50% to fall 50%

$$\text{Duty cycle} = \left(\frac{t_w}{T} \right) 100\%$$

Basically describes how long wave is at HIGH value
 t_w = pulse width

Only three basic logic operations:

- NOT

 

- AND



- OR



Fixed Function IC's

1. Dual in-line package (DIP):
 - cheapest
2. Small-outline IC (SOIC):
 - Flatter pins
 - Thinner
 - Easier to fit
3. Flat pack (FP)
 - Pins can be bent/cut
 - Used in aerospace
 - Withstand higher temps
4. Plastic-leaded chip carrier (PLCC)
 - J connections pins
 - Compact
 - More pin out for a given area
5. Leaded-ceramic chip carrier (LCCC)
 - Occupies less space
6. Ball Grid Array (BGA)
 - Identical pattern on board
 - Heat solder balls - melt and connect

Data Representation


16 October 2016 18:44

- Information can be represented by a voltage level
- The simplest information is TRUE/FALSE
 - This can be represented by two voltage levels:
 - 5 Volts for TRUE
 - 0 Volts for FALSE
- A voltage signal which has only two possibilities is a BIT
 - Bit stands for **B**inary **D**igit
- Binary means: only 2 possible values

FALSE	TRUE
(0)	(1)

- Advantages of using binary representation
 - simple to implement in electronic hardware (switch)
 - good tolerance to noise

Digital - Great Noise Immunity

 

Q# Format

2^4	2^3	2^2	2^1	2^0	2^{-1}	2^{-2}	2^{-3}
1	0	0	1	1	0	1	1

Binary Point

$(19.375)_{10}$

This 8-bit number is in Q3 format
– 3 bits after the binary point

Conversions:

• Decimal to Binary:

$$\begin{aligned} 50_{10} &= 32 + 18 \\ &= 32 + 16 + 2 \\ &= 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^1 \\ 50_{10} &= 110010_2 \end{aligned}$$

• Binary to Decimal:

- eg: Convert $(1101)_2$ into decimal
- $1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = (13)_{10}$

Binary Addition - Right to Left

- $0 + 0 = 0$ carry-out 0
- $0 + 1 = 1$ carry-out 0
- $1 + 0 = 1$ carry-out 0
- $1 + 1 = 0$ carry-out 1
- $1 + 1 + \text{carry-in} = 1$ carry-out 1

Hexadecimal Numbers conversions

Binary-to-hexadecimal conversion

1. Break the binary number into 4-bit groups
2. Replace each group with the hexadecimal equivalent

Hexadecimal-to-decimal conversion

1. Convert the hexadecimal to groups of 4-bit binary
2. Convert the binary to decimal
3. Or, convert directly using powers of 16

Decimal-to-hexadecimal conversion

- Repeated division by 16

Binary Coded Decimal (BCD)

- Use 4-bit binary to represent one decimal digit
- Easy conversion
- Wasting bits (4-bits can represent 16 different values, but only 10 values are used)
- Used extensively in financial applications

Grey Code: Only 1 bit changes in increasing count sequence

ASCII - 7-bit

Basic Logic Gates & Boolean Expressions

13 November 2016 18:05

● = AND

+ = OR


Order of Precedence:

- Single term inversions
- parenthesis
- **AND before OR**
- Expression Inversions

To build gates

- Block1
 - Two transistors in series
- Block2
 - Two transistors in //
- NMOS - Active HIGH
- PMOS - Active LOW

Start from *logic-circuit diagram*

 

Boolean Algebra

13 November 2016 18:06

Laws

Commutative

- $A + B = B + A$
- $A \bullet B = B \bullet A$

Associative

- $A + (B + C) = A + B + C$
- $A \bullet (B \bullet C) = A \bullet B \bullet C$

Distributive

- $A(B + C) = AB + AC$

Rules of Boolean Algebra

- $A + 0 = A$
- $A + 1 = 1$
- $A \cdot 0 = 0$
- $A \cdot 1 = A$
- $A + A = A$
- $A + \bar{A} = 1$
- $A \cdot A = A$
- $A \cdot \bar{A} = 0$
- $\bar{\bar{A}} = A$
- **$A + AB = A$**
- **$A + \bar{A}B = A + B$**
- **$(A + B)(A + C) = A + BC$**

DeMorgan's theorem:

Switch to invert of single variables

Add or remove Bar

Change operator

- $\overline{(X + Y)} = \bar{X} \cdot \bar{Y}$
 - $X + Y = \overline{(\bar{X} \cdot \bar{Y})}$
- $\overline{(X \cdot Y)} = \bar{X} + \bar{Y}$
 - $X \cdot Y = \overline{(\bar{X} + \bar{Y})}$

Universality

GATE	NAND	NOR
INV	All inputs same	All inputs same
AND	Output of first- Both input of 2nd	Invert inputs Feed into NOR
OR	Invert inputs Feed into NAND	Output of first- Both input of 2nd

Alternate Gate Representation Steps

1. Invert inputs and output of gate
2. Change Boolean Operator
 - a. Except for inverter

Aim to match input and outputs

- Bubble to bubble
- Non-bubble to non-bubble

Logic Simplification & Karnaugh Map

13 November 2016 18:06

Sum of Products - AND terms into an OR gate

Product of Sums - OR terms into an AND gate

Canonical Form - every variable appears in every term

SOP to Canonical

- Term missing variable X
 - AND with $(X + \bar{X})$

Can use $f[\square] = \sum()$ to express Canonical

Sum of PRODUCTS

Number inside ()

Represents row number from truth table

Variables inside []

ORDER matters

Logic Simplification

Method 1: Algebra

Things to try

- Grouping
 - Factorisation
- Multiplication by redundant variables
 - Multiply term without X by:
 - $X + \bar{X}$
 - $1 + X$
 - Doesn't alter logic
- Apply DeMorgan's theorem
 - Useful for expressions with lots of inversions

Method 2: Karnaugh Maps

Normally works by filling in table with a SOP expression

Grey code ordering

Avoid with more than 4 variables

- With 5, use two maps, and group over 3D

1. Find pairs
2. Group - use minimum number of groups
 - a. X - don't care - treat as 0 or 1 for min groups
3. New SOP formed

Can be done to POS expressions as well

1. Group 0's to produce a SOP
2. Make a POS with same terms from above
3. Apply DeMorgan's theorem to each term

More Gates and their Applications

13 November 2016 18:07

XOR gate - HIGH when only 1 input is HIGH



XOR used for **selectable inversion**

When B HIGH, A inverted

When B LOW, A normal



XNOR gate - HIGH when inputs are same - inverted XOR

XNOR used in **PARITY** generator and checker

Other Representation

Input on left

Output on the right

Common inputs on top control block

If numbered

- Only perform action when asserted
- With corresponding input/output in lower blocks

Label	Name
EN	Enable
G	AND
V	OR
N	Invert
S	Set
R	Reset

Multiplexer

- Select inputs select one of the Data inputs for output
 - **# Data inputs = $2^{\text{\# select lines}}$**
- Each input is **AND'd with all select lines**
- **Output = OR of all the above terms**

Implementing Logic in a MUX

- Select lines = Variables
- Data inputs connected to GND or +Vcc depending on Output of combination of variables
 - GND if output should be 0
 - +Vcc if output should be 1
 - Check from Truth Table

Demultiplexer

- Only one Data input
- Select lines choose which output(s) to send input to
- # Outputs = $2^{\text{\# Select lines}}$
- Implement:
 - Data line is AND'd with all combinations of select lines
 - Each output comes from each AND gate

Signed Numbers & Arithmetic Circuits

13 November 2016 18:08

2's Compliment

- Invert and add 1
- MSB has weighting of -1
- Can use adder circuits to perform subtraction
 - Can use unsigned Adder HW

Sign Extension

- Duplicate Sign-bit into new MSB's

Add 2 n-bit Signed numbers and avoid overflow

- Sign extend to **n+1 bits**
- Use n+1 bit adder

Multiply a signed number by -1

- Invert and +1
- Doesn't work for smallest number

LSR	Divide by 2
LSL	Multiply by 2
ASR	Signed Divide by 2

Half-Adder

- Sum = A XOR B
- Carry = AB

Full-Adder

- Sum = A XOR M
 - M = B XOR Cin
- C = OR of:
 - AB
 - ACin
 - BCin
- From 2 Half-Adders
 - First produces HSum and HCarry
 - Second:
 - Sum = HSum + Cin
 - Carry = HCarry OR SecondCarry

Parallel Adder

- One Full-Adder per bit
- Carry out from bit n = Carry in for bit n+1

Propagation delay = n x delay for one adder

To make this Subtract

- Set **first Carry in = 1**
- **Invert bits** for Number to be subtracted

Comparators

- Output HIGH when **corresponding bits equal**
- Use a **XNOR** gate

To extend to N-bits

- Use XNOR gates for each pair of bits
- **AND the XNOR outputs**

Decoders

- Binary Decoder
 - Output for Decimal value is only Asserted when inputs match binary representation of the decimal value
- Also Have:
 - BCD - Decimal
 - BCD - 7-Segment

ROM & Programmable Logic Devices

31 March 2017 02:48

Memory Cell - stores 1-bit

To Address ROM - $A \times B$

A = number of cells

B = word length

$$2^N = A$$

N = number of control lines

Half for row

Half for columns

Implementing Logic

N # of Inputs

B # of Outputs

From Truth Table, most right variable = LSB input

ROM cell

MOS transistor for switch

Row control line set to as signal for Transistor

When row line asserted, all row cells release stored value to respective columns

PLD's

Implement canonical SOP expressions

Reduces chip count

Static hazards

0 hazard: 0 -1 -0

1 hazard: 1-0-1

In K-Map, groups that do not overlap are potential HAZARDS

- To avoid, add group that overlaps
- Redundant logic, but prevents hazard

Flip-flops

31 March 2017 02:48

Three main types

- Reset - Set (RS / SC)
- JK
- D


Clock Edge

- If **Bubble** on CLK input
 - Negative-going transition
- Hold input stable**
 - On clock edge
 - Setup time Before edge
 - Hold Time After edge
 - Allows Sequential FF

Asynchronous Inputs

- Asserted **CLEAR** - $Q = 0$
- Asserted **PRESET** - $Q = 1$
- Both Asserted - normal operation


NAND Gate Latch: Set - Reset

 

ACTIVE LOW

Set	Reset	Output
1	1	No Change
0	1	$Q = 1$
1	0	$Q = 0$
0	0	INVALID

NOR Gate Latch: Set - Reset

 


ACTIVE HIGH

Set	Reset	Output
0	0	No Change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	INVALID

To make FF clocked,

- Use **edge detector** circuit -> CLK*
- AND** CLK* with S/R
 - Use these as inputs for S R in circuit

J-K Flip-flop

 


J(S)	K(R)	CLK	Q
0	0		No Change
1	0		1
0	1		0
1	1		Toggle

D Flip-Flop

- Same as JK but only two possible inputs


D	Q
0	0
1	1

Clocked D FF

 

D Latch - Enable signal

 - EN = 0: Q is latched to its value
- EN = 1: $Q = D$ - D passes through



EN	D	Q
0	X	Q_0
1	0	0
1	1	1

State Diagrams

31 March 2017 02:49

Moore Model

State Diagram

- Circle for each state
 - Inside circle:
 - State Number - starting from 1
 - Associated Output
 - e.g. 1/0 - State #1, output = 0
- Arrows for each transition between states
 - Label with required inputs
 - e.g. 11 - A = 1, B = 1

State Table

- One Row for each State
- Input Columns in Grey code order

Assigned State Table

- Output associated with that state
- Replaces the state in the table
- Same contents as a K-MAP
 - Row is Present Output
 - Next Output = Boolean Expression

Mealy Model

State Diagram

- More useful when output depends on inputs, not previous state
- **Circles - only labelled with state number**
- Arrow Labels
 - Inputs / Next Output
 - e.g. 10/1 - input of 1 and 0 gives output of 1


Circuits Using Flip-flops

04 April 2017 13:35

Register

- Parallel D FF's
- Global RESET line

Shift Register

 


Serial FF

Q connected to next D input

- Can input **Serial data at D0**
 - Wait **N cycles to shift data N-bits**
- **Parallel port to load // data**
 - **1 cycle to shift by 1-bit**

Divide **CLK** by 2

Connect \bar{Q} to D

 

Asynchronous Counter

- String together Divide by 2 circuits
- Previous \bar{Q} is next FF CLK
- Take Q as bit output

Low Max Clock Freq

- Can be used to divide CLK by a power of 2

Synchronous Counter

- FF store value
- Use separate Adder to Increment / Decrement

Finite State Machines

04 April 2017 13:35

FSM By Combinatorial Logic

1. Start with Transition Table of FF used
2. Construct State Transition Table
3. K-Map for each Output of CL block, from its inputs
4. Extract Boolean Expressions from K-Maps
5. Can use X for don't cares or map to a base state

FSM By ROM

1. Cells Contain State Outputs
2. Use current State as Address
 - a. Cell pointed to contains next State

Using Shift Register for a DELAY

- D Input Synchronous
 - Q0 delayed by 1 cycle
 - QN delayed by 1 + N cycles
 -
- D Input Asynchronous
 - Q0 delayed by UP TO 1 cycle = T_0
 - QN delayed by $T_0 + N$ cycles

Two States are considered Equivalent if

- Have same next state
- Have same current output

IF removing a state from diagram, ensure no undefined State

- Make it redundant and point to Base state no matter input