

Introduction

12 October 2016 14:40

Assume 0 resistance in circuit diagram wires

When charge is free to move, every point in the circuit is electrically neutral

Node - all the points that are connected together with interconnecting wires in a circuit
A node has 0 resistance so the voltage is the same everywhere along the node

Arrow of current on wire does not matter.

If outcome is -ve then current is flowing in opposite direction to the arrow

Branches - Components that link a pair of nodes

Passive sign convention - make voltage arrow opposite to current arrow

Conductance = 1/ resistance

Any node is chosen to be grounded and is referenced to 0V

$$V_{AB} = V_A - V_B$$

When current flows through a resistor, electrical potential energy > heat energy

$P = V.I$ for any component

On Graph

$P = V^2/R = I^2.R$ - **only for resistors**

When taking in energy, $V.I > 0$
When supplying energy, $V.I < 0$

In any circuit, the **net power will sum to zero**, as elements are supplying and absorbing the same amount overall.

Quantity	Letter	Unit	Symbol
Charge	Q	Coulomb	C
Conductance	G	Siemens	S
Current	I	Amp	A
Energy	W	Joule	J
Potential	V	Volt	V
Power	P	Watt	W
Resistance	R	Ohm	Ω

Value	Prefix	Symbol
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f

Value	Prefix	Symbol
10^3	kilo	k
10^6	mega	M
10^9	giga	G
10^{12}	tera	T
10^{15}	peta	P


results (2015-7003) Introduction: 1 - 15 / 16

Resistor Circuits

12 October 2016 15:08

KVL - the sum of the voltages around any closed loop is zero

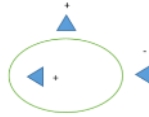KCL - the sum of the currents entering and exiting any closed loop always sums to zero



Entering loop	-ve
Exiting loop	+ve


Series:

To spot - each internal node connects to only two branches
Same current flowing through resistors


Parallel:

To spot - components are connected to the same pair of nodes
Same voltage across each resistor

Notation: $3||7 = \frac{1}{\frac{1}{3} + \frac{1}{7}} = 2.1$

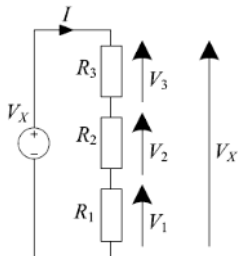


Voltage Divider

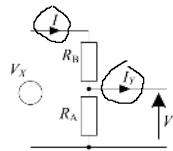

If $I_Y = 0$ then voltage divider works as normal
If I_Y is much smaller than I , then voltage divider approximately works.

V_X is divided into $V_1 : V_2 : V_3$ in the proportions $R_1 : R_2 : R_3$.

Current Divider

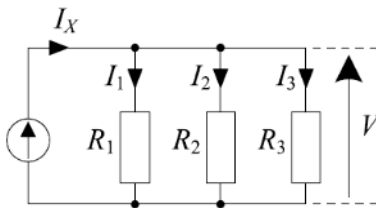

Special case for **TWO** resistors - works like a VD

$$I_1 = \frac{R_2}{R_1 + R_2} I_X$$

I_X is divided into $I_1 : I_2 : I_3$ in the proportions $G_1 : G_2 : G_3$.

$$= 1/R_1 : 1/R_2 : 1/R_3$$

Equivalent Resistors

- Does not affect relationship between V and I
- Series:
 - Nodes disappear
- Parallel:
 - Currents disappear
 - Number of nodes stays the same

Parallel Resistors - Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

These formulae work for any number of resistors.

- For the special case of two parallel resistors


$$R_P = \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \text{ ("product over sum")}$$

- If one resistor is a multiple of the other

Suppose $R_2 = kR_1$, then

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{k R_1^2}{(k+1) R_1} = \frac{k}{k+1} R_1 = \left(1 - \frac{1}{k+1}\right) R_1$$

Internal Resistance

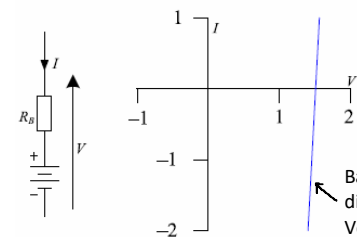

$$V = V_B + I R_B$$


Battery is discharging here - Voltage decreases as current draw increases

Nodal Analysis

Always label one node as 0V at start

For a circuit with N nodes and S voltage sources, there will always be N - S - 1 KCL simultaneous equations to solve.

Weighted Average Circuit:

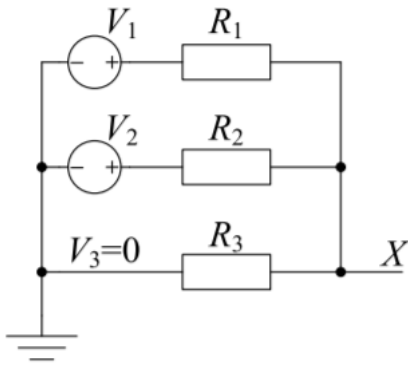

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

$$X(G_1 + G_2 + G_3) = V_1G_1 + V_2G_2 + V_3G_3$$

$$X = \frac{V_1G_1 + V_2G_2 + V_3G_3}{G_1 + G_2 + G_3} = \frac{\sum V_i G_i}{\sum G_i}$$

Voltage X is the average of V_1 , V_2 , V_3 weighted by the conductances.

Universal Nodal Analysis Algorithm:

- Pick any node as 0V, label dependant sources as V_s and I_s
- Label nodes next to known voltage sources
- Label any unlabelled nodes with X, Y.. And create super nodes with these terms if any exist
- For any dependent sources, write down an equation in terms of known nodes/ values
- Write down KCL equations for all nodes - include super nodes in normal node KCL's
- Solve simultaneous equations

Summary of Nodal Analysis:

- Simple Circuits (no floating or dependent voltage sources)
- Floating Voltage Sources
 - ▷ use supernodes: all the nodes connected by floating voltage sources (independent or dependent)
- Dependent Voltage and Current Sources
 - ▷ Label each source with a variable
 - ▷ Write extra equations expressing the source values in terms of node voltages
 - ▷ Write down the KCL equations as before

Screen clipping taken: 13/11/2016 16:16

Linearity and Superposition


12 November 2016 11:04

Linearity theorem - Any circuit containing resistors and independent voltage and current sources,
Every node voltage and branch current is a linear function of the source values


EG -

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$

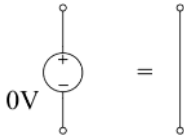Zero Value Voltage source - short circuit



Zero Value Current source - open circuit

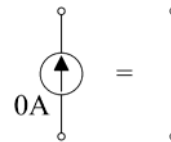

Superposition - set all but one of the independent sources to 0, and find value of node in terms of one source. Repeat for all sources, then add $X_1, X_2, X_3 \dots$ to get X

Power DOES NOT obey superposition

If there are dependent sources, treat as independent then eliminate from final expressions

Proportionality - If all **independent** sources are multiplied by a value K , then all voltages and currents in the circuit will be multiplied by the value K , and the power dissipated by any component will be multiplied by K^2

Thevenin and Norton Equivalents

12 November 2016 11:04

Norton - CURRENT SOURCE - PARALLEL

Thevenin - VOLTAGE SOURCE - SERIES

NCP _ TVS

Thevenin Properties:

- $V = R_{TH}I + V_{TH}$
- Open circuit, $I = 0$, then $V_{OC} = V_{TH}$
- Short circuit, $V = 0$, then $I_{SC} = -V_{TH} / R_{TH}$
- R_{TH} is represented by $1 / \text{slope}$ of IV graph

Norton Properties:

- $I = V / R_{TH} - I_{VO}$
- Open circuit, $I = 0$, then $V_{OC} = I_{NO}R_{TH}$
- Short circuit, $V = 0$, $I_{SC} = -I_{NO}$
- $R_{NO} = R_{TH}$

To find Thevenin Resistance:

- Voltage sources - short circuit
- Current source - open circuit
- Then find resistance between the two terminals

Thevenin via nodal analysis:

1. Label ground as output terminal
2. Write down nodal equations
3. Eliminate all nodes except for input terminal node

Small R_{TH}	Large R_{TH}
Thevenin	Norton

Change between Norton and Thevenin -	$V_{TH} = I_{NO}R_{TH}$	Just like $V=IR$
--------------------------------------	-------------------------	------------------

Power Transfer from an equivalence circuit, connected to a resistance L .

For a fixed R_{TH} , max power transferred when $R_{TH} = R_L$

Operational Amplifiers

12 November 2016 11:04

Negative feedback adjusts output Y to make $V_+ \sim V_-$


Positive Feedback - $V_{OUT} = \pm V_{MAX}$

To analyse Op-Amp circuit


- Assume $A \sim \infty$
- Assume 0A input current

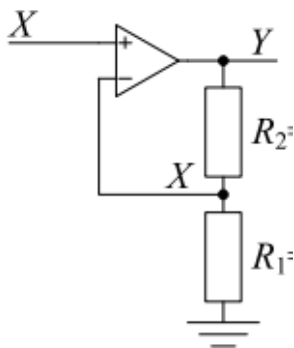1. Check for negative feedback, Y connected somehow to V_-
2. Assume $V_+ = V_-$
3. Apply KCL at each input separately, with input current 0

Non-inverting Amplifier $Y/X = 1 + R_2 / R_1$




Inverting Amplifier $Y/X = -R_2 / R_1$

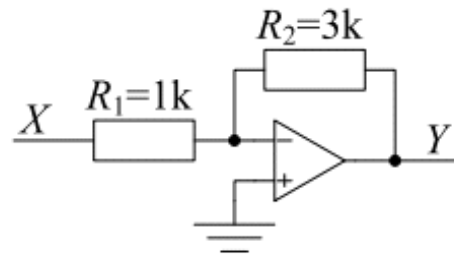

Inverting Summing Amp

Y is **weighted sum** of input voltages X_i

Where coefficient is $-R_F / R_i$

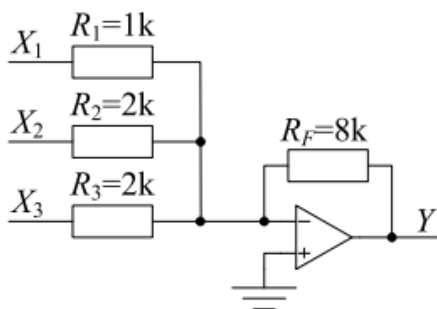

Differential Amp

Output = $A(\text{Input 1} - \text{Input 2})$


So proportional to the difference

Use superposition to work out A


Block Diagrams

13 November 2016 18:04

Gain Block: $V = U \times A$

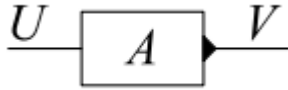

Adder Block: $Q = P_1 + P_2 - P_3$

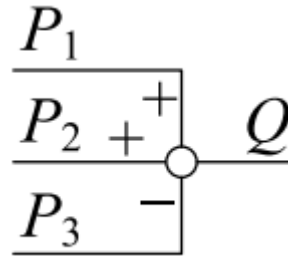

To solve block diagrams:

1. **Label** all inputs, outputs and adder outputs
2. Write down **equations** for the **output** and all **adder outputs**
3. **Solve** by eliminating unwanted variables


Nonlinear Components

13 November 2016 18:04

A diode

To solve a circuit with a diode, guess how it acts, then check if condition is correct

Region	Condition	Equation	Acts as
Forward Bias (On)	$I > 0$	$V = 0$	Short Circuit
Reverse Bias (Off)	$V < 0$	$I = 0$	Open Circuit
	Check this after	Make the guess	

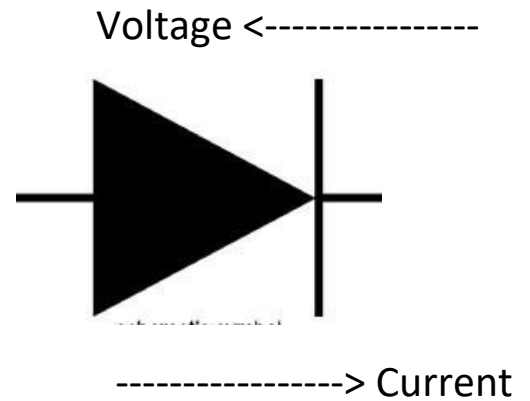


For real diode, switching occurs around 0.7V

Can high-current circuits, $V \sim 1.0V$

Bridge Rectifier (Full wave)

4 Diodes,

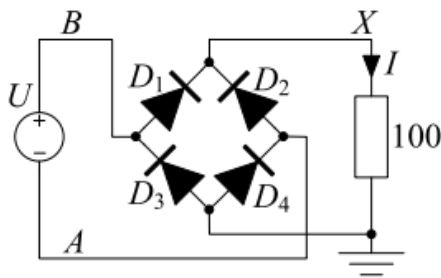

2 cases:

- D_1 and D_4 on
- D_2 and D_3 on

$$X = |U|$$

If U is AC, then X has double its frequency

Halfwave Rectifier

- Gives $X = \max(U - 0.7, 0)$
- U causes Diode to switch on and off

U	Diode	X
< 0.7	OFF	0
≥ 0.7	ON	$U - 0.7$

Precision Halfwave Rectifier

- Gives $X = \max(U, 0)$
- Use of op-amps eliminates the 0.7V diode drop

Capacitors and Inductors

13 November 2016 18:04

Capacitor Equations:

$$q = Cv$$

differentiate both sides w.r.t. t:

$$i = C \frac{dv}{dt}$$

-> voltage doesn't change instantly

$$W = \frac{1}{2} Cv^2$$

Inductor Equations:

$$v = L \frac{di}{dt}$$

-> current doesn't change instantly

$$W = \frac{1}{2} LI^2$$

AVERAGE power absorbed by these components = **0**

As energy stored is returned over time

	<u>Series</u>	<u>Parallel</u>
<u>Capacitor</u>	// EQN for R	SUM capacitance
<u>Inductor</u>	SAME as R	SAME as R

Can tell from Circuit Symbols

Capacitor	Inductor
Average CURRENT = 0	Average Voltage = 0

Sine waves and Phasors

13 November 2016 18:04

Phasor: A complex number representing a sin wave

The sine wave:

$$A \cos(2\pi ft + \phi) = \underline{A \cos \phi} \cos 2\pi ft + \underline{A \sin \phi} \sin 2\pi ft = \underline{X} \cos 2\pi ft + \underline{Y} \sin 2\pi ft$$

$$\begin{array}{lcl} \text{Phasor } V & = & X + jY \\ \text{Wave } v(t) & = & X \cos 2\pi ft - Y \sin 2\pi ft \end{array}$$

- Plus j in phasor > Minus sine in wave
- Assume Frequency is known

Complex number $X + jY$ represents the sine wave at time $t = 0$;

Magnitude of a phasor = $\sqrt{X^2 + Y^2}$, gives the Amplitude of the sine wave

Argument of a phasor = $\tan^{-1} \frac{Y}{X}$, gives Phase Shift relative to $\cos 2\pi ft$

Phase Shift	Relative to $\cos 2\pi ft$
<0	Lagging
>0	Leading

Phasor Arithmetic

Operation	Phasor
ADDITION	$V_1 + V_2$
SCALING	aV
DIFFERENTIATE	$j\omega V$

Complex Impedance

Component	Z
Resistor	R
Inductor	$j\omega L$
Capacitor	$\frac{1}{j\omega C}$

CIVIL

In a Capacitor I leads V but V leads I in an Inductor

For any network (resistors+capacitors+inductors):

(1) Impedance = Resistance + $j \times$ Reactance

$$Z = R + jX (\Omega)$$

(2) Admittance = $\frac{1}{\text{Impedance}}$ = Conductance + $j \times$ Susceptance

$$Y = \frac{1}{Z} = G + jB \text{ Siemens (S)}$$

$$\text{So } G = \frac{R}{R^2 + X^2} = \frac{R}{|Z|^2}$$

$$B = \frac{-X}{R^2 + X^2} = \frac{-X}{|Z|^2}$$

Beware: $G \neq \frac{1}{R}$ unless $X = 0$.

Frequency Responses

08 January 2017 19:03

Transfer function of the circuit is $\frac{\text{output}}{\text{input}} = \text{gain of the circuit}$

Phasor input into any RCL circuit gives Phasor output, which **varies with input frequency** of input phasor

Voltage ratio in decibels (dB) = $20 \log_{10} \frac{|V_2|}{|V_1|}$

Have to **plot two graphs** for output,

- **|Gain| vs ω**
- **Phase vs ω**

For $H = C(j\omega)^R$

- Magnitude response
 - **C is the y-intercept**
 - **R is the gradient of the straight line**
- Phase response
 - **Horizontal line**
 - **Phase = $90^\circ \times R$**
 - **If $C < 0$, $\pm 180^\circ$**

BEFORE AND AFTER straight line approximations can be found without factorisation:

- **Low Freq. Asymptote**
 - $\frac{\text{Lowest power of } j\omega \text{ from top}}{\text{Lowest power of } j\omega \text{ from bottom}}$
- **High Freq. Asymptote**
 - $\frac{\text{Highest power of } j\omega \text{ from top}}{\text{Highest power of } j\omega \text{ from bottom}}$

To plot Magnitude Response for any Transfer function, $H(j\omega)$

- **Factorize the polynomials**
- Find **Corner Frequencies**
 - $(j\omega + \alpha)$
- Do approximations as straight line **before, between and after corner frequencies**
 - For frequency less than corner frequency - factor becomes an ω
 - Higher factors become their constant terms

To plot Phase Response for any Transfer function, $H(j\omega)$

- **Factorize the polynomials after HF and LF**
- Find **Corner Frequencies**
 - $(j\omega + \alpha)$
 - Take note if from Numerator or Denominator
- If from Denominator
 - At $0.1\omega_c$, Plot decreases by -45° rad/decade
 - At $10\omega_c$, Plot increases by $+45^\circ$ rad/decade
- If from Numerator
 - At $0.1\omega_c$, Plot increases by $+45^\circ$ rad/decade
 - At $10\omega_c$, Plot decreases by -45° rad/decade
- For **Intermediate horizontal straight-line** section
 - Value = $\text{previous horizontal} \pm \frac{\pi}{4} \log_{10} \left(\frac{\text{current corner freq}}{\text{previous corner freq}} \right)$

Resonance

08 January 2017 19:04

Occurs when quadratic factor in transfer function cannot be factorised into linear factors

Resonant Frequency, ω_r , occurs when Impedance, Z, is purely real

- Current in L and C cancel out

For Quadratic factor $F(j\omega) = A(j\omega)^2 + B(j\omega) + C$

- $\omega_c = \sqrt{\frac{C}{A}}$
- Damping factor, $\zeta = \frac{B}{\sqrt{4AC}} = \frac{B \cdot \text{Sgn}(A)}{2A\omega_c}$
- Quality Factor, $Q \approx \frac{1}{2\zeta}$
- $Q \triangleq \omega \times W_{\text{stored}} \div \bar{P}_R$
 - $W_{\text{stored}} = \text{peak stored energy}$
 - $\bar{P}_R = \text{average power loss through resistor}$

Half-power bandwidth

- Gain² (power)
 - Range of frequencies
 - For which power is greater than half its peak

Magnitude Plot:

- Small ζ > higher peak, smaller bandwidth
- Large ζ > lower peak at lower ω_p , larger bandwidth
 - Peak Frequency, $\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$
 - True for circuit with only one quadratic factor in denominator

Phase Plot:



- Small ζ > faster phase change around ω_c

Filters

08 January 2017 19:04


Order of a circuit = highest power of (jw) in the denominator of the Transfer function

	Low	High
Capacitor	Open Circuit	Short Circuit
Inductor		

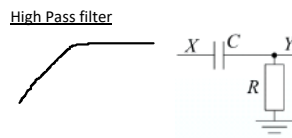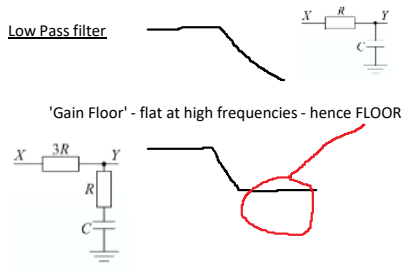

Integrator
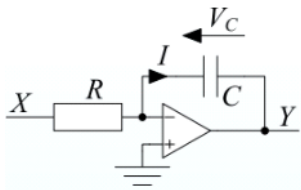
$$\frac{Y}{X} = - \frac{1}{j\omega C} \frac{1}{R}$$



Op-Amp Filter advantages:

- Can have gain > 1
- Low output impedance
- Input impedance does not vary with frequency

Filter Transformations

Impedance Scaling by factor K

R'	C'	L'
KR	$K^{-1}C$	KL

Frequency Shift - To the LEFT by a factor of K

R'	C'	L'
R	KC	KL

LR to RC circuit

$$\square R' = KL$$

$$\square C' = \frac{1}{KR}$$

Reflection in Frequency axis around ω_m

$$\square R' = \frac{K}{\omega_m C}$$

$$\square C' = \frac{1}{\omega_m KR}$$

- Magnitude plot flips
- Phase plot flips and NEGATES

Power in AC

08 January 2017 19:04

$$\langle y \rangle = \frac{1}{T} \int_0^T y dt$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt$$

$$V_{rms} \triangleq \sqrt{\langle v^2(t) \rangle} \equiv DC \text{ voltage}$$

For Voltage phasor $V = |V|e^{j\theta_1}$ and Current phasor $I = |I|e^{j\theta_2}$

$$\text{Average Power, } P = \frac{1}{2} |V||I| \cos(\theta_1 - \theta_2)$$

Power Factor of V and I is $\cos(\theta_1 - \theta_2)$

Complex Power

- $S = \text{RMS Voltage} * \text{RMS Conjugate Current}$
- $S = \tilde{V} * \tilde{I}^* = \frac{|\tilde{V}|^2}{Z^*} = |\tilde{I}|^2 * Z$
- $S = P + jQ = |\tilde{V}||\tilde{I}| \cos \phi + |\tilde{V}||\tilde{I}| \sin \phi$
- Phase of S = Phase of Z
- Apparent Power = |Complex|
- $\text{Real}(S) = \text{Average Power} = P$
- $\text{Imaginary}(S) = \text{Reactive Power} = Q$
- $\cos \phi = \frac{P}{|S|}$
- Capacitors generate Reactive Power
- Inductors absorb Reactive Power
- Phase of S = Phase of Z
- Complex Power in any **circuit** = 0 - Tellegen's Theorem

Transients

08 January 2017 19:05

$$y(t) = y_{ss}(t) + y_{Tr}(t)$$

$y_{ss}(t)$ **same frequency as new input**

Use **nodal/Phasor analysis** to get this term

$y_{Tr}(t)$ if of the form $Ae^{-t/\tau}$

Does not depend on input, only the circuit

$$\tau = RC \text{ or } \frac{L}{R}$$

A depends on initial conditions of input

- RC - find $v_C(0-)$, RL - find $i_L(0-)$
 - Find $y(0+)$ via Nodal Analysis or other
 - $A = y(0+) - y_{ss}(0+)$
- Can work out R_{Th}
 - Remove C or L when working out R_{Th}

Sinusoidal input

- For y_{ss}
 - Get transfer Function
 - $y_{ss}(t) = X * H(w)$

Negative Exponential

Time it takes to get somewhere from a known point

$$T = \tau * \ln\left(\frac{\text{initial distance to Limit}}{\text{final distance to Limit}}\right)$$

Transient from Transfer Function:

- Calculate $H(w)$
- $y_{ss}(t) = \text{LF gain} * x(t)$
- $y(\text{discontinuity}) = \text{HF gain} * x(\text{discontinuity})$
- $\tau = \frac{1}{\text{Denominator CF}}$
- Then work out A using difference



Transmission Lines

08 January 2017 19:05

Transmission Line Equations

- $C_0 \frac{\partial v}{\partial t} = -\frac{\partial i}{\partial x}$

- Capacitance per unit length, $C_0 = \frac{C}{\partial x}$

- $L_0 \frac{\partial i}{\partial t} = -\frac{\partial v}{\partial x}$

- Total Inductance per unit length, $L_0 = \frac{L_1 + L_2}{\partial x}$

SOLUTIONS

- $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$

- $i(t, x) = \frac{f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)}{Z_0}$

- u is the propagation delay

- $Z_0 = \sqrt{\frac{L_0}{C_0}}$

Power Flow into region

- $P = \frac{f^2}{Z_0} - \frac{g^2}{Z_0}$

- f carries power into the region
- g carries power out of the region

Driving a Line:

Voltage on line is from potential divider of Driver Resistance and Z_0

Reflections

Backwards wave is a multiple of forward wave

$$g_L = \rho_L f_L$$

Reflection Coefficient

$$\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$$

ρ	Comment
0	No Reflection
+1	Open Circuit - Double Voltage
-1	Closed Circuit - 0V

TL and Phasors

05 April 2017 21:09

f and g are sinusoidal with same frequency

$F_0 = Ae^{j\phi}$ - Phasor at start of line

At point x on the line:

$$k = \frac{\omega}{u}$$

- $F_x = F_0 e^{-jkx}$
- $G_x = G_0 e^{+jkx}$

At Load, L

- Ohms Law applies
- ρ_L still same
- Travelling from x to L

- $e^{-jk(L-x)}$ is the phase delay
 - ^ Multiply Phasor by this

Reflections - Creates a Standing Wave

- Amplitude of Line Voltage $\propto X$
- Max Amplitude of $(1 + |\rho_L|)$ occurs every $\frac{\lambda}{2}$ away from L